


# EECS 316

## Computer Design



### LECTURE 4:


## The VHDL N-bit Adder

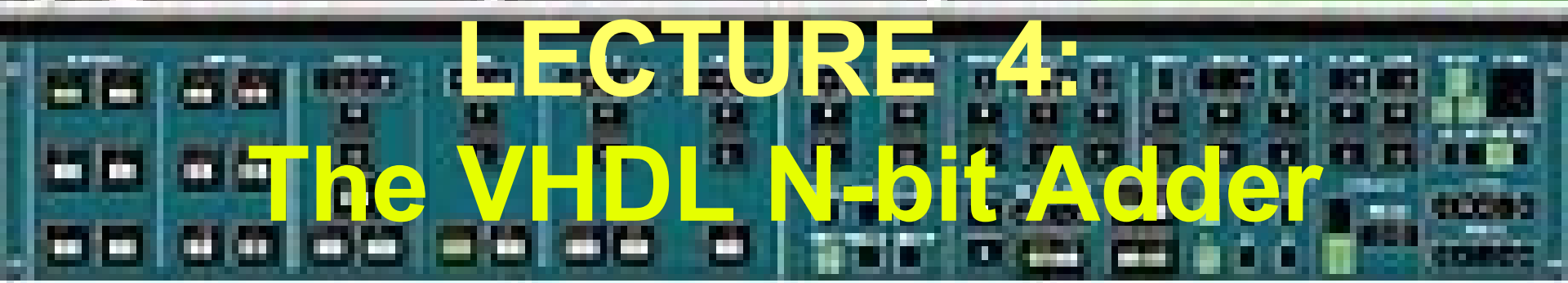

*Instructor: Francis G. Wolff*  
*wolff@eecs.cwru.edu*

*Chris Papachristou*  
*Case Western Reserve University*

# Review: N-Bit Ripple-Carry Adder

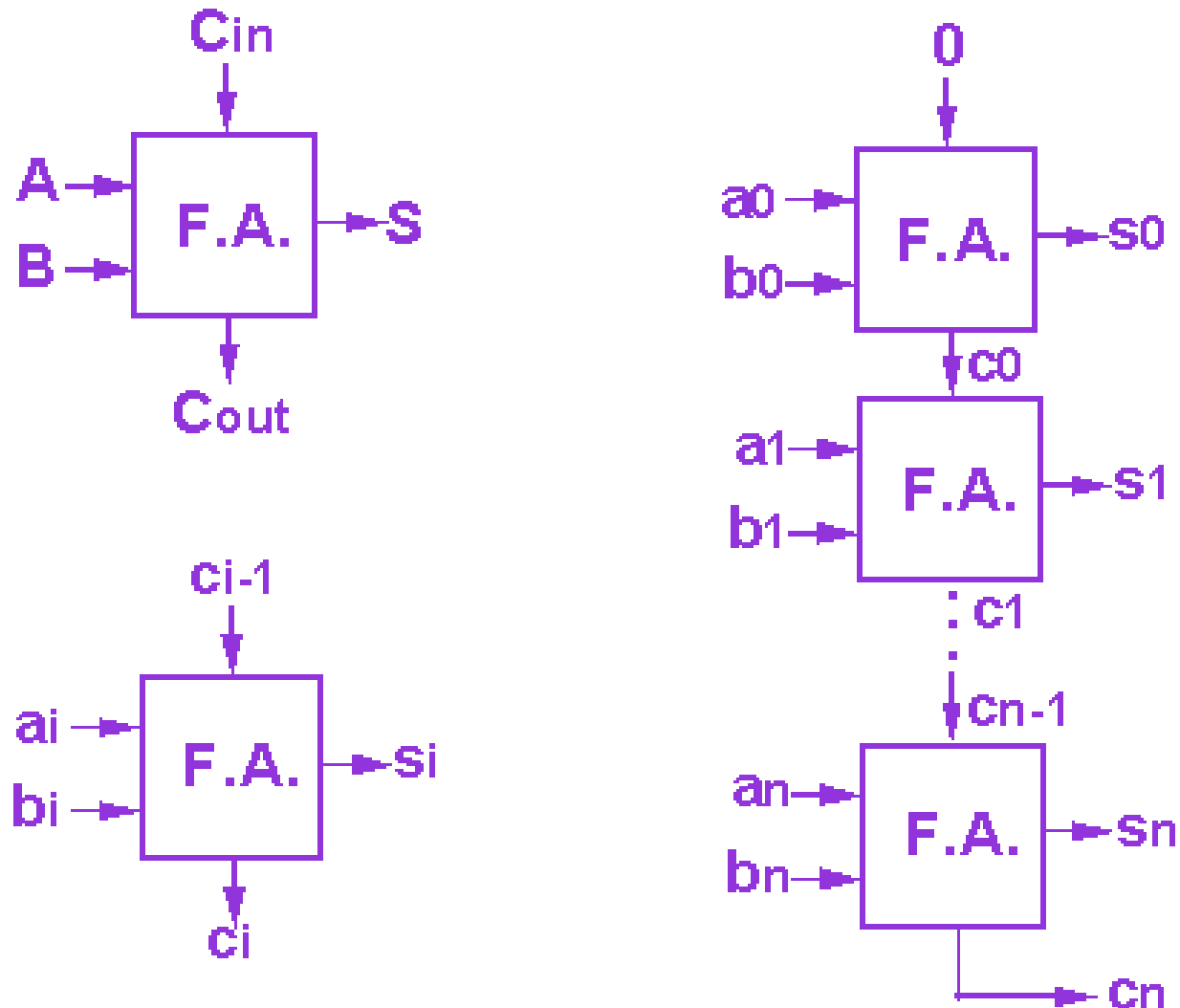

# Hierarchical design: 2-bit adder



- The design interface to a two bit adder is

```
LIBRARY IEEE;  
USE IEEE.std_logic_1164.ALL;  
  
ENTITY adder_bits_2 IS  
    PORT (Cin:          IN    std_logic;  
          a0, b0, a1, b1: IN    std_logic;  
          S0, S1:       OUT   std_logic;  
          Cout:         OUT   std_logic  
    ); END;
```

- Note: that the ports are **positional dependant**  
(Cin, a0, b0, a1, b1, S0, S1, Cout)

# Hierarchical design: Component Instance



## Component Declaration

```
ARCHITECTURE ripple_2_arch OF adder_bits_2 IS
  COMPONENT full_adder
    PORT (x, y, z: IN std_logic; Sum, Carry: OUT std_logic);
  END COMPONENT;
  SIGNAL t1: std_logic;
BEGIN
  FA1: full_adder PORT MAP (Cin, a0, b0, S0, t1);
  FA2: full_adder PORT MAP (t1, a1, b1, s1, Cout);
END;
```

Component instance #1 called FA1

Component instance #2 called FA2

# Positional versus Named Association



- **Positional Association** (must match the port order)

FA1: full\_adder PORT MAP (Cin, a0, b0, S0, t1);

- **Named Association**: signal => port\_name

FA1: full\_adder PORT

MAP (Cin=>x, a0=>y, b0=>z, S0=>Sum, t1=>Carry);

FA1: full\_adder PORT

MAP (Cin=>x, a0=>y, b0=>z, t1=>Carry, S0=>Sum);

FA1: full\_adder PORT

MAP (t1=>Carry, S0=>Sum, a0=>y, b0=>z, Cin=>x);

# Component by Named Association



ARCHITECTURE **ripple\_2\_arch** OF **adder\_bits\_2** IS

COMPONENT **full\_adder**

PORT (**x, y, z**: IN std\_logic; **Sum, Carry**: OUT std\_logic);

END COMPONENT;

SIGNAL **t1**: std\_logic; -- Temporary carry signal

BEGIN

-- Named association

FA1: **full\_adder** PORT

MAP (**Cin=>x, a0=>y, b0=>z, S0=>Sum, t1=>Carry**);


-- Positional association

FA2: **full\_adder** PORT MAP (**t1, a1, b1, s1, Cout**);

END;

-- Comments start with a double dash


# Using vectors: std\_logic\_vector



```
ENTITY adder_bits_2 IS
  PORT (Cin:          IN  std_logic;
        a0, b0, a1, b1: IN  std_logic;
        S0, S1:       OUT std_logic;
        Cout:         OUT std_logic
  ); END;
```

- By using **vectors**, there is less typing of variables, a0, a1, ...
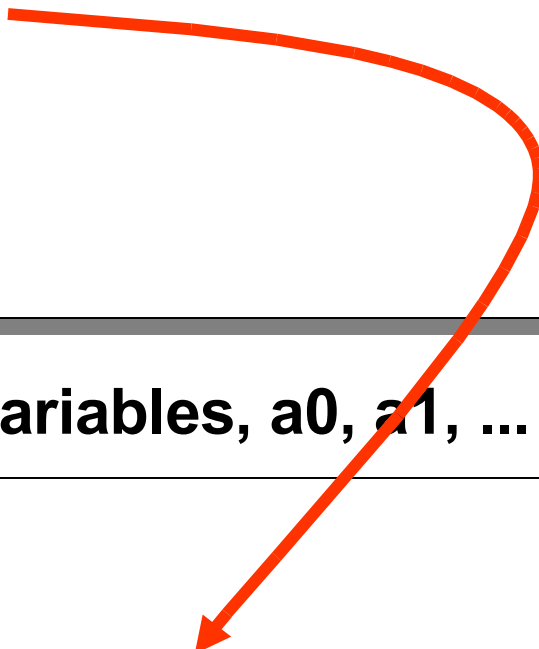
```
ENTITY adder_bits_2 IS
  PORT (Cin:          IN  std_logic;
        a, b:         IN  std_logic_vector(1 downto 0);
        S:            OUT std_logic_vector(1 downto 0);
        Cout:         OUT std_logic
  ); END;
```




# 2-bit Ripple adder using std\_logic\_vector

- Note, the signal variable usage is now different:  
**a0 becomes a(0)**

```
ARCHITECTURE ripple_2_arch OF adder_bits_2 IS
    COMPONENT full_adder
        PORT (x, y, z: IN std_logic; Sum, Carry: OUT std_logic);
    END COMPONENT;
    SIGNAL t1: std_logic; -- Temporary carry signal
BEGIN
    FA1: full_adder PORT MAP (Cin, a(0), b(0), S(0), t1);

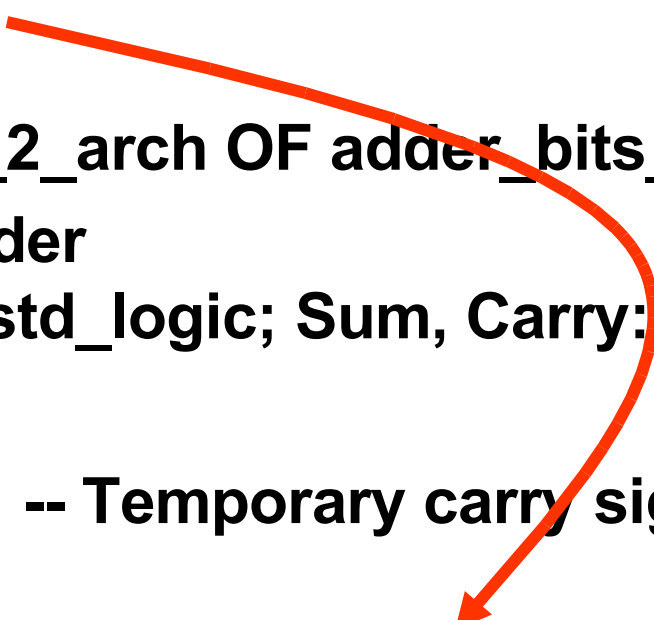    FA2: full_adder PORT MAP (t1, a(1), b(1), s(1), Cout);
END;
```





# 4-bit Ripple adder using std\_logic\_vector



ARCHITECTURE ripple\_4\_arch OF adder\_bits\_4 IS

COMPONENT full\_adder

PORT (x, y, z: IN std\_logic; Sum, Carry: OUT std\_logic);

END COMPONENT;

SIGNAL t: std\_logic\_vector(3 downto 1);

BEGIN

FA1: full\_adder PORT MAP (Cin, a(0), b(0), S(0), t(1));

FA2: full\_adder PORT MAP (t(1), a(1), b(1), S(1), t(2));

FA3: full\_adder PORT MAP (t(2), a(2), b(2), S(2), t(3));

FA4: full\_adder PORT MAP (t(3), a(3), b(3), S(3), Cout);

END;

- std\_vectors make it easier to replicate structures

# For-Generate statement: **first improvement**



ARCHITECTURE **ripple\_4\_arch** OF **adder\_bits\_4** IS

COMPONENT full\_adder

PORT (**x, y, z**: IN std\_logic; **Sum, Carry**: OUT std\_logic);

END COMPONENT;

SIGNAL **t**: std\_logic\_vector(3 downto 1);

CONSTANT **n**: INTEGER := 4;

BEGIN

Constants never change value

FA1: full\_adder PORT MAP (**Cin, a(0), b(0), S(0), t(1)**);

**FA\_f: for i in 1 to n-2 generate**

**FA\_i: full\_adder PORT MAP (t(i), a(i), b(i), S(i), t(i+1));**

**end generate;**

FA4: full\_adder PORT MAP (**t(n), a(n), b(n), S(n), Cout**);

END;

LABEL: before the for is **not** optional

# For-Generate statement: **second improvement**



ARCHITECTURE **ripple\_4\_arch** OF **adder\_bits\_4** IS

COMPONENT **full\_adder**

PORT (**x, y, z**: IN std\_logic; **Sum, Carry**: OUT std\_logic);

END COMPONENT;

SIGNAL **t**: std\_logic\_vector(4 downto 0);

CONSTANT **n**: INTEGER := 4;

BEGIN

**t(0)** <= **Cin**;      **Cout** <= **t(n)**;

FA\_f: for **i** in 0 to **n-1** generate

FA\_i: **full\_adder** PORT MAP (**t(i), a(i), b(i), S(i), t(i+1)**);

end generate;

END;



Keep track of vector sizes

# N-bit adder using **generic**

```
ENTITY adder_bits_4 IS
```

```
    PORT (Cin:      IN    std_logic;
          a, b:      IN    std_logic_vector(3 downto 0);
          S:         OUT   std_logic_vector(3 downto 0);
          Cout:      OUT   std_logic
```

```
); END;
```

- By using **generics**, the design can be generalized

```
ENTITY adder_bits_n IS
```

```
    GENERIC(n:INTEGER := 2);
```

```
    PORT (Cin:      IN    std_logic;
```

```
          a, b:      IN    std_logic_vector(n-1 downto 0);
```

```
          S:         OUT   std_logic_vector(n-1 downto 0);
```

```
          Cout:      OUT   std_logic
```

```
); END;
```

Default case is 2

# For-Generate statement: **third improvement**



```
ARCHITECTURE ripple_n_arch OF adder_bits_n IS
  COMPONENT full_adder
    PORT (x, y, z: IN std_logic; Sum, Carry: OUT std_logic);
  END COMPONENT;
  SIGNAL      t:      std_logic_vector(n downto 0);
BEGIN
  t(0)  <= Cin;      Cout <= t(n);
  FA: for i in 0 to n-1 generate
    FA_i: full_adder PORT MAP (t(i), a(i), b(i), S(i), t(i+1));
  end generate;
END;
```

# Stimulus Only Test Bench Architecture

ARCHITECTURE adder\_bits\_4\_tb\_arch OF adder\_bits\_4\_tb IS

COMPONENT **adder\_bits\_n**

GENERIC(**n**: INTEGER := 2);

PORT (**Cin**: IN std\_logic;

**a, b**: IN std\_logic\_vector(n-1 downto 0);

**S**: OUT std\_logic\_vector(n-1 downto 0);

**Cout**: OUT std\_logic

END COMPONENT;

SIGNAL **x, y, Sum**: std\_logic\_vector(**n** downto 0);

SIGNAL **c, Cout**: std\_logic;

BEGIN

**x** <= "0000", "0001" after 50 ns, "0101", after 100 ns;

**y** <= "0010", "0011" after 50 ns, "1010", after 100 ns;

**c** <= '1', '0' after 50 ns;

**UUT\_ADDER\_4**: **adder\_bits\_n** GENERIC MAP(4)

PORT MAP (**c, x, y, Sum, Cout**);

END;

MAP(4)  
Overrides  
default 2

# Stimulus Only Test Bench Entity



```
ENTITY adder_bits_4_tb IS
```


```
    PORT (Sum:      std_logic_vector(3 downto 0);
```

```
          Cout:    std_logic
```

```
); END;
```

The output of the testbench will be observe by the digital waveform of the simulator.

# Review: 1-bit Tri-State buffer

 

```
ENTITY TriStateBuffer IS
    PORT(x:      IN      std_logic;
          y:      OUT     std_logic;
          oe:     IN      std_logic
    ); END;
```

ARCHITECTURE Buffer3 OF TriStateBuffer IS  
BEGIN


```
WITH oe SELECT
y <=  x  WHEN '1', -- Enabled
      'Z' WHEN OTHERS; -- Disabled
```

OTHERS includes 0,  
W, X, L, H, U cases

END;



# N-bit Tri-State Buffer entity

 

**ENTITY TriStateBufferN IS**


**GENERIC(**  $n$ : **INTEGER** := 8);

**PORT (**  $x$ : **IN**  $\text{std\_logic\_vector}(n-1 \text{ downto } 0$ ;  
 $y$ : **OUT**  $\text{std\_logic\_vector}(n-1 \text{ downto } 0$ );  
 $oe$ : **IN**  $\text{std\_logic}$ );

**);**


**END;**

# N-bit Tri-State Buffer architecture

 

```
ARCHITECTURE TriStateBufferN_ARCH OF TriStateBufferN IS
  COMPONENT TriStateBuffer
    PORT (x: IN std_logic; y: OUT std_logic, oe: IN std_logic);
  END COMPONENT;
BEGIN
  TB: FOR i IN 0 TO n-1 GENERATE
    TB_i: TriStateBuffer PORT MAP (x(i), y(i), oe);
  END GENERATE;
END;
```

# ROM: 4 byte Read Only Memory

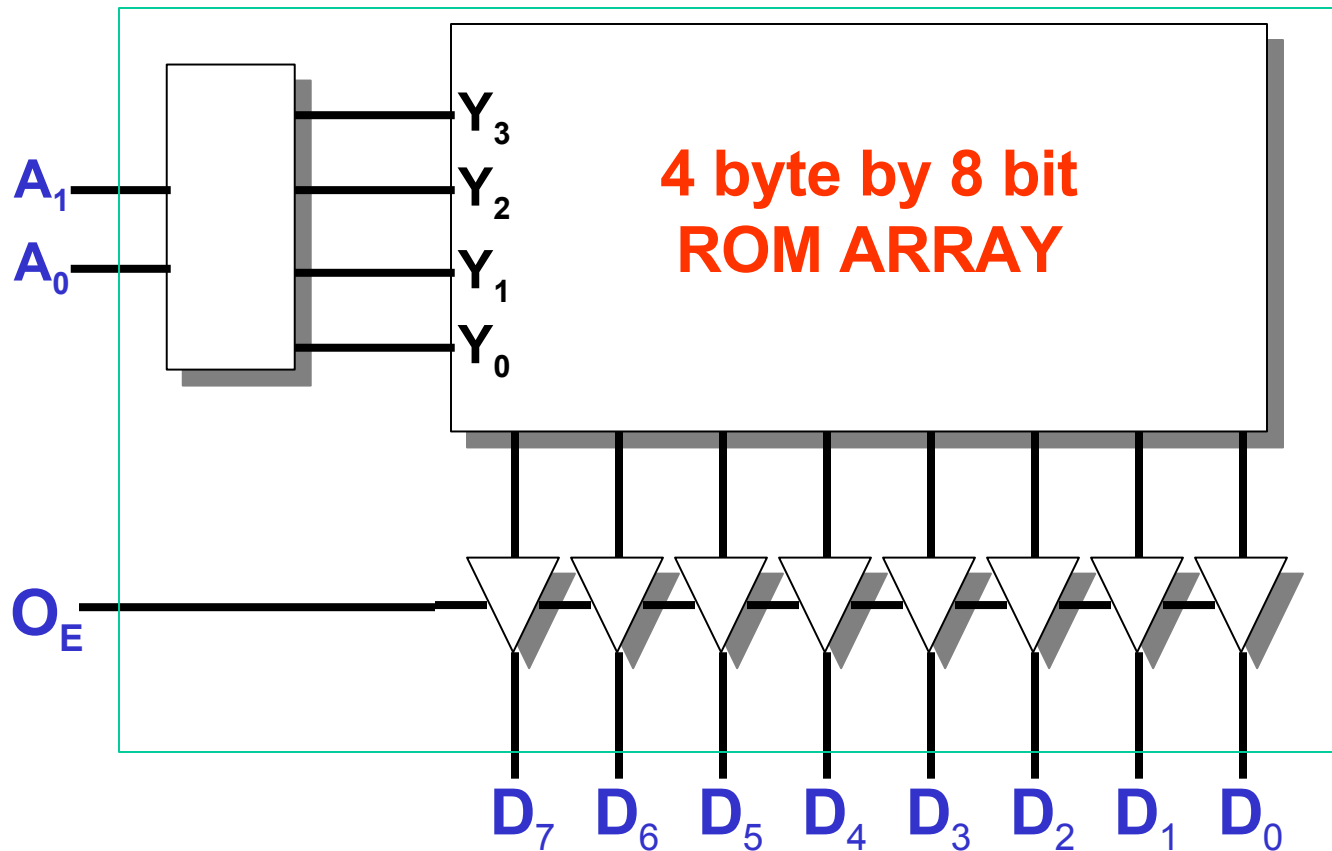

ENTITY **rom\_4x8** IS

PORT(**A**: IN std\_logic\_vector(1 downto 0);

**OE**: IN std\_logic;

**D**: OUT std\_logic\_vector(7 downto 0)); END;

# ROM: 4 byte Read Only Memory

ARCHITECTURE **rom\_4x8\_arch** OF **rom\_4x8** IS

**COMPONENT** TriStateBufferN

**GENERIC**(n: **INTEGER** := 1);

**PORT** (  
    **x**: **IN**            **std\_logic\_vector**(n-1 downto 0);  
    **y**: **OUT**           **std\_logic\_vector**(n-1 downto 0);  
    **oe**: **IN**  **std\_logic**);

**END COMPONENT**;

**SIGNAL** **ROMout**: **std\_logic\_vector**(7 downto 0);

**BEGIN**

**BufferOut**: TriStateBufferN **GENERIC** MAP(8)



**PORT** MAP(**ROMout**, **D**, **OE**);

**WITH** **A** **SELECT**

**ROMout** <= "01000001" **WHEN** "00",  
              "11111011" **WHEN** "01",  
              "00000110" **WHEN** "10",  
              "00000000" **WHEN** "11";

**END**;

# Review: 2-to-1 & Datapath Multiplexor

  

**Datapath is n bits wide**

WITH **s** SELECT


**Y** <= **a** WHEN '0',  
**b** WHEN OTHERS;

WITH **s** SELECT

**Y** <= **a** WHEN '0',  
**b** WHEN OTHERS;

**Where is the difference?**
 
# Generic 2-to-1 Datapath Multiplexor Entity



```
LIBRARY IEEE;  
USE IEEE.std_logic_1164.all;
```

```
ENTITY Generic_Mux IS  
    GENERIC (n: INTEGER);  
    PORT (Y: OUT std_logic_vector(n-1 downto 0);  
          a: IN  std_logic_vector(n-1 downto 0);  
          b: IN  std_logic_vector(n-1 downto 0);  
          S: IN  std_logic_vector(0 downto 0)  
    );  
END ENTITY;
```

# Generic 2-to-1 Datapath Multiplexor Architecture



ARCHITECTURE **Generic\_Mux\_arch** OF **Generic\_Mux** IS  
BEGIN

    WITH **S** SELECT

**Y** <= **a** WHEN "1",

**b** WHEN OTHERS;

END ARCHITECTURE;

CONFIGURATION **Generic\_Mux\_cfg** OF **Generic\_Mux** IS  
  FOR **Generic\_Mux\_arch**  
  END FOR;  
END CONFIGURATION;

Configurations are  
required for simulation

# VHDL Component, Entity, and Architecture

for-generate | if generate

Component Instance

Component Declaration

Entity

Architecture<sub>i</sub>

Concurrent  
Boolean  
Equations

Concurrent  
With-Select-When  
When-Else

Other  
Concurrent  
Components



# Summary of VHDL Components



## Component Declaration

[ Optional ] { repeat }

**COMPONENT** **component\_entity\_name**

[ **GENERIC** ( { **identifier**: **type** [ := **initial\_value** ]; } ) ]

[ **PORT** ( { **identifier**: **mode type**; } ) ]

**END**;

Add ; only if another identifier

## Component Instance

**identifier** : **component\_entity\_name**

[ **GENERIC MAP** ( **identifier** { , **identifier** } ) ]

[ **PORT MAP** ( **identifier** { , **identifier** } ) ]

;

**mode** := **IN** | **OUT** | **INOUT**

**type** := **std\_logic** | **std\_logic\_vector**(**n downto 0**) | **bit**

# Assignment #4



a) Write an N-bit ALU (default N=8) using the vhdl code of assignment #3 and then run (N=8) using **vhdlan** and **vhdl sim assigns**. The initial carry-in is set to zero and the final carry out is not needed. The N-bit ALU should only have x(n), y(n), s(n) and f. For multiple bits (i.e. std\_logic\_vector) use:

assign "00101111" Y                      #binary

or

assign X"2f" Y                      #hex notation

Write a **one** useful test case for **each** function. **Make sure it gives the correct results (i.e. please debug your ALU)!** Hand in the source files and session using the Unix script command.

b) Write an 8-bit ALU test bench in VHDL and hand in the source files and session using the Unix script command.