

EECS 317 Computer Design




LECTURE 6: State machines

Instructor: Francis G. Wolff
wolff@eecs.cwru.edu

Chris Papachristou
Case Western Reserve University

Gated-Clock SR Flip-Flop (Latch Enable)

 

$Q \leq (S \text{ NAND } LE) \text{ NAND } \overline{Q};$

$\overline{Q} \leq (R \text{ NAND } LE) \text{ NAND } Q;$

Synchronous terminology:
Set and Reset


Asynchronous terminology:
Preset and Clear

Latches require that during the gated-clock the data must also be stable (i.e. S and R) at the same time

Suppose each gate was 5ns: **how long does the clock have to be enabled to latch the data?**

Answer: 15ns

Structural SR Flip-Flop (Latch)

 

NAND		
R	S	Q_{n+1}
0	0	U
0	1	1
1	0	0
1	1	Q_n


ENTITY **Latch** IS

 PORT(R, S: IN std_logic; Q, NQ: OUT std_logic);
END ENTITY;

ARCHITECTURE **latch_arch** OF **Latch** IS
BEGIN

 Q <= R NAND NQ;
 NQ <= S NAND Q;
END ARCHITECTURE;

 Inferring Behavioral Latches: Asynchronous



NAND		
R	S	Q_{n+1}
0	0	U
0	1	1
1	0	0
1	1	Q_n


Sensitivity list of signals:
Every time a change of state or event occurs on these signals this process will be called

ARCHITECTURE `Latch2_arch` OF `Latch` IS
BEGIN

```
PROCESS (R, S) BEGIN
  IF R= '0' THEN
    Q <= '1'; NQ<='0';
  ELSIF S='0' THEN
    Q <= '0'; NQ<='1';
  END IF;
END PROCESS;
END ARCHITECTURE;
```

Sequential Statements

Gated-Clock SR Flip-Flop (Latch Enable)

 

ARCHITECTURE **Latch_arch** OF **GC_Latch** IS BEGIN
PROCESS (R, S, LE) BEGIN

IF **LE**='1' THEN

IF **R**= '0' THEN

Q <= '1'; **NQ**<='0';

ELSIF **S**='0' THEN

Q <= '0'; **NQ**<='1';


END IF;

END IF;

END PROCESS;

END ARCHITECTURE;

Rising-Edge Flip-flop

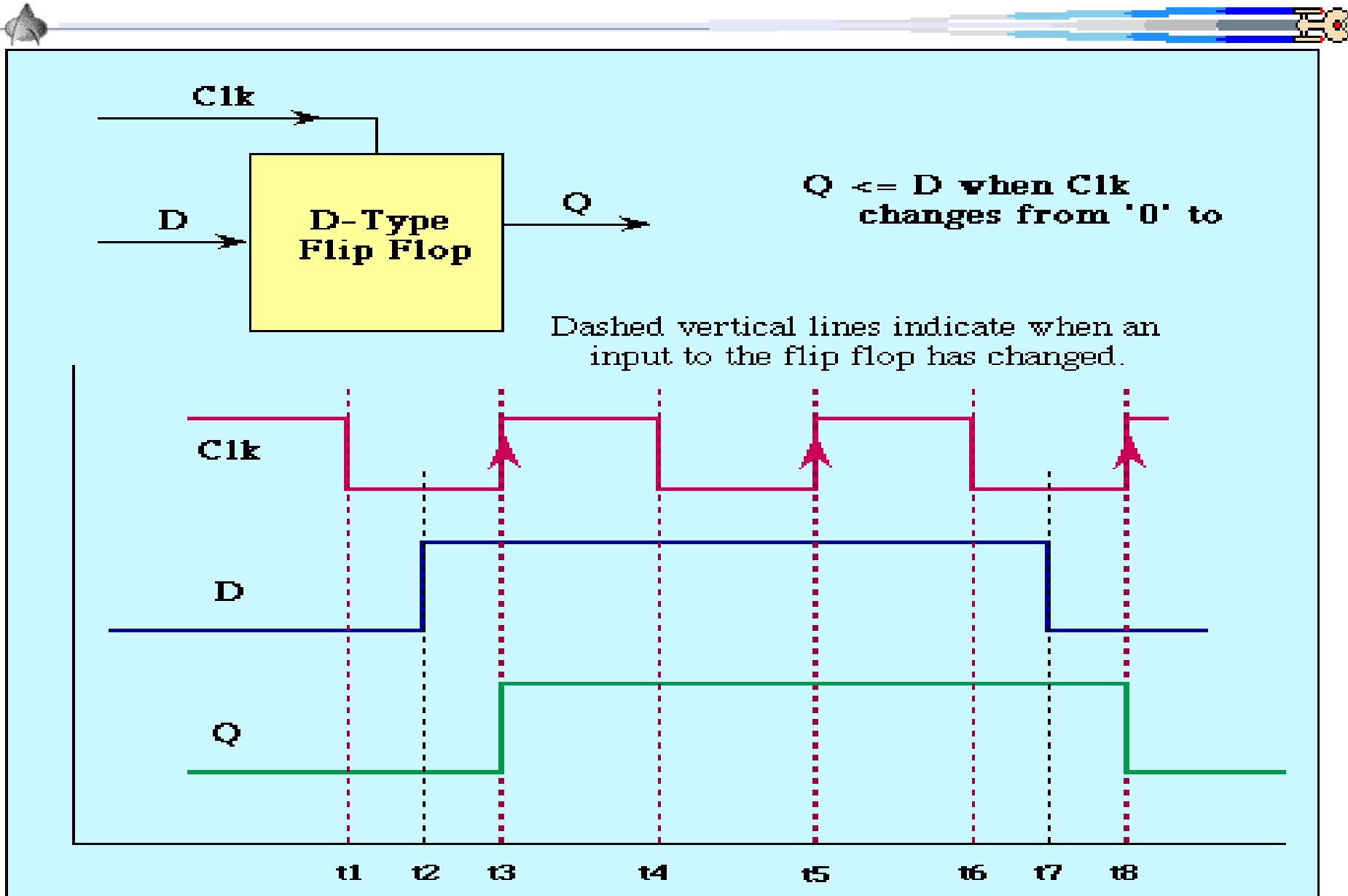



EECS 316

Inferring D-Flip Flops: Synchronous

ARCHITECTURE Dff_arch OF Dff IS
BEGIN

```
PROCESS (Clock) BEGIN
    IF Clock'EVENT AND Clock='1' THEN
        Q <= D;
    END IF;
END PROCESS;
END ARCHITECTURE;
```

Notice the Process
does not contain D:
PROCESS(Clock, D)

Sensitivity lists contain
signals used in
conditionals (i.e. IF)

Clock'EVENT is what
distinguishes a D-
FlipFlip from a Latch

Inferring D-Flip Flops: rising_edge



```
ARCHITECTURE Dff_arch OF Dff IS BEGIN
  PROCESS (Clock) BEGIN
    IF Clock'EVENT AND Clock='1' THEN
      Q <= D;
    END IF;
  END PROCESS;
END ARCHITECTURE;
```

Alternate and more readable way is to use the rising_edge function

```
ARCHITECTURE dff_arch OF dff IS BEGIN
  PROCESS (Clock) BEGIN
    IF rising_edge(Clock) THEN
      Q <= D;
    END IF;
  END PROCESS;
END ARCHITECTURE;
```

Inferring D-Flip Flops: Asynchronous Reset



```
ARCHITECTURE dff_reset_arch OF dff_reset IS BEGIN
```

```
    PROCESS (Clock, Reset) BEGIN
```

```
        IF Reset= '1' THEN -- Asynchronous Reset
```

```
            Q <= '0'
```

```
        ELSIF rising_edge(Clock) THEN --Synchronous
```

```
            Q <= D;
```

```
        END IF;
```

```
    END PROCESS;
```

```
END ARCHITECTURE;
```

Inferring D-Flip Flops: Synchronous Reset

```
PROCESS (Clock, Reset) BEGIN
    IF rising_edge(Clock) THEN
        IF Reset='1' THEN
            Q <= '0'
        ELSE
            Q <= D;
        END IF;
    END IF;
END PROCESS;
```

Synchronous Reset
Synchronous FF

```
PROCESS (Clock, Reset) BEGIN
    IF Reset='1' THEN
        Q <= '0'
    ELSIF rising_edge(Clock) THEN
        Q <= D;
    END IF;
END PROCESS;
```



Asynchronous Reset
Synchronous FF

D-Flip Flops: Asynchronous Reset & Preset



```
PROCESS (Clock, Reset, Preset) BEGIN
    IF Reset='1' THEN --highest priority
        Q <= '0';
    ELSIF Preset='1' THEN
        Q <= '0';
    ELSIF rising_edge(Clock) THEN
        Q <= D;
    END IF;
END PROCESS;
```

VHDL clock behavioral component

 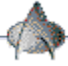


```
ENTITY clock_driver IS
    GENERIC (Speed: TIME := 5 ns);
    PORT (Clk: OUT std_logic);
END;
```

```
ARCHITECTURE clock_driver_arch OF clock_driver IS
    SIGNAL Clock:      std_logic := '0';
BEGIN
    Clk <= Clk XOR '1' after Speed;
    Clock <= Clk;
END ARCHITECTURE;
```

```
CONFIGURATION clock_driver_cfg OF clock_driver IS
    FOR clock_driver_arch END FOR;
END CONFIGURATION;
```

Synchronous Sequential Circuit

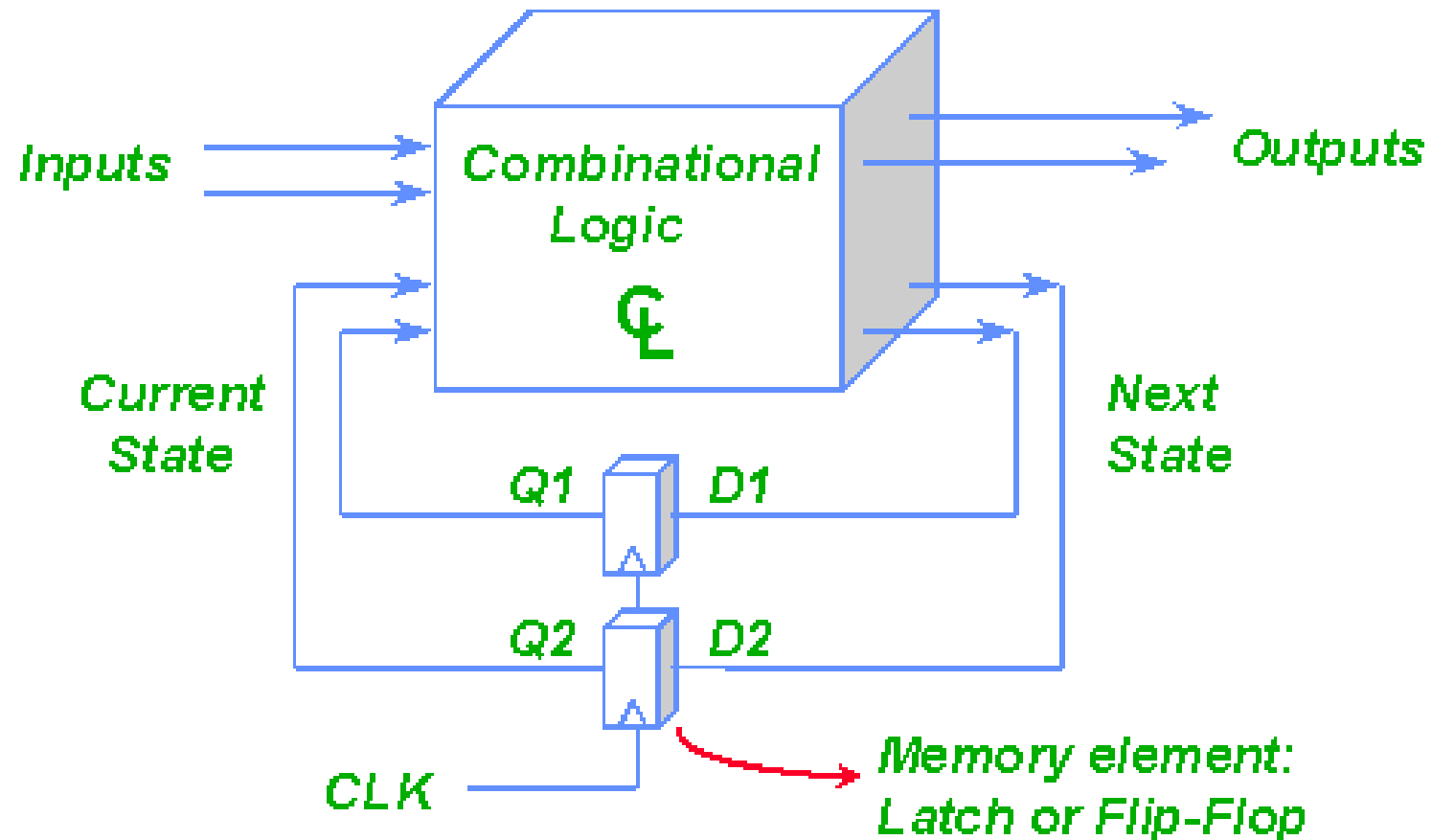


Issues: Specification, design, clocking and timing

Abstraction: Finite State Machine

- A Finite State Machine (FSM) has:
 - **K** states, $S = \{s_1, s_2, \dots, s_K\}$, initial state s_1
 - **N** inputs, $I = \{i_1, i_2, \dots, i_N\}$
 - **M** outputs, $O = \{o_1, o_2, \dots, o_M\}$
 - Transition function $T(S, I)$ mapping each current state and input to a next state
 - Output function $O(S)$ mapping each current state to an output
- Given a sequence of inputs the FSM produces a sequence of outputs which is dependent on s_1 , $T(S, I)$ and $O(S)$

FSM Representations

State Transition Graph

 

	t	$t+1$	$t+2$
Inputs:	0	1	0
Outputs:	00	<u> </u>	

State Transition Table

$T(S, I)$


0	s_1	s_2
1	s_1	s_3
0	s_2	s_1
1	s_2	s_2
0	s_3	s_1
1	s_3	s_3

$O(S)$


s_1	00
s_2	10
s_3	11

Moore Machines

 - So far we considered Moore machines where the output O is a function of only the current state Q




- Moore FSM State Transition Graph

 

Simple Design Example

 - Design a FSM that outputs a 1 if and only if the number of 1's in the input sequence is odd



ENTITY **FSM_Parity** IS

PORT (**i1**:

IN std_logic;

o1:

OUT std_logic;

CLK:

IN std_logic; --Clock

RST:


IN std_logic --Reset

); END;

– *State Encoding is sequentially done by VHDL*

TYPE **FSMStates** IS (**s1**, **s2**); --s1=0, s2=1

 SIGNAL **State**, **NextState**: **FSMStates**;



- **State Encoding**: Choose a unique binary code for each s_i so the combinational logic can be specified

- Choose $s_1 = 0$ and $s_2 = 1$

- Choose $s_1 = 1$ and $s_2 = 0$

– *The non-sequential case requires the following*

ATTRIBUTE FSMencode: string;

ATTRIBUTE FSMencode of **FSMStates**: TYPE IS "1 0";

Simple Design Example

```
PROCESS (State, i1) BEGIN
```

```
  CASE State IS
```


```
    WHEN s1 => if i1='1' then NextState <= s2;  
                else NextState <= s1; end if;
```

```
    WHEN s2 => if i1='1' then NextState <= s1;  
                else NextState <= s2; end if;
```

```
    WHEN OTHERS => NextState <= NextState;
```

```
  END CASE;
```

```
END PROCESS;
```

 

FSM Controller: Current State Process



ARCHITECTURE FSM_Parity_arch OF FSM_Parity IS

TYPE FSMStates IS (s1, s2);

SIGNAL State, NextState: FSMStates;

BEGIN

PROCESS (State, i1) BEGIN

CASE State IS

WHEN s1 => if i1='1' then NextState <= s2;
else NextState <= s1; end if;

WHEN s2 => if i1='1' then NextState <= s1;
else NextState <= s2; end if;

WHEN OTHERS => NextState <= NextState;

END CASE;

END PROCESS;

WITH State SELECT

o1 <= '0' WHEN s1,
'1' WHEN s2,
'1' WHEN OTHERS; -- X, L, W, H, U

Alternative: less coding



```
ARCHITECTURE FSM_Parity_arch OF FSM_Parity IS
  TYPE    FSMStates IS (s1, s2);
  SIGNAL  State, NextState: FSMStates;
BEGIN
```

```
  PROCESS (State, i1) BEGIN
```

```
    CASE State IS
```

```
      WHEN s1 =>    if i1='1' then    NextState <= s2;
                    else              NextState <= s1;
                    end if;
```

```
      o1 <= '0';
```

```
      WHEN s2 =>    if i1='1' then    NextState <= s1;
                    else              NextState <= s2;
                    end if;
```

```
      o1 <= '1';
```

```
      WHEN OTHERS =>
```

```
        o1 <= '1'; NextState <= NextState;
```

```
    END CASE;
```

```
  END PROCESS;
```

Important Note:
every input to
the state
machine must be
in the PROCESS
sensitivity list

**Important
Note:** every
WHEN must
assign the
same set of
signals: i.e.
NextState
and o1. if you
miss one
assignment
latches will
show up!

FSM controller: NextState Process



```
PROCESS (CLK, RST) BEGIN
```

```
    IF RST='1' THEN -- Asynchronous Reset
```

```
        State <= s1;
```

```
    ELSIF rising_edge(CLK) THEN
```

```
        State <= NextState;
```

```
    END IF;
```

```
END PROCESS;
```

```
END ARCHITECTURE;
```

```
CONFIGURATION FSM_Parity_cfg OF FSM_Parity IS
```

```
    FOR FSM_Parity_arch
```

```
        END FOR;
```

```
END CONFIGURATION;
```


Choose $s_1 = 0$ and $s_2 = 1$

Q I

i_1	Q	D
0	0	0
1	0	1
0	1	1
1	1	0

Q II


Q	o_1
0	0
1	1

 

Choose $s_1 = 1$ and $s_2 = 0$


i_1	Q	D
0	1	1
1	1	0
0	0	0
1	0	1

Q	o_1
1	0
0	1

 

Coke Machine Example

 
- Coke costs \$.10
- Only nickels and dimes accepted
- FSM inputs:
 - 5: Nickel
 - 10: Dime
 - Coke: Give me a coke
 - Return: Give me my money back
- FSM outputs:
 - Drop: Drop a coke
 - Ret5: Return \$.05
 - Ret10: Return \$.10



Coke Machine State Diagram


Assumption: At most one input among **Coke**, **5**, **10**, and **Return** is asserted

 * represents all unspecified transitions from state



Does this work? _____

Coke Machine Diagram - II

 

After **Return** input, any input in the next cycle is ignored!

Assignment #6



- a) Write the VHDL synchronous code (**no latches!**) and test bench for the coke II machine. Note: the dc_shell synthesis analyze command will tell you if you inferred latches. Hand code and simulation using the Unix script command.
- b) Synthesize the your design and hand in the logic diagram, Unix script include cell, area, timing report.