

EECS 316

Computer Design

LECTURE 2:

Delay models, std_ulogic,
with select when

Instructors: Francis G. Wolff

wolff@eecs.cwru.edu

Chris Papachristou

cap2@cwru.edu

Case Western Reserve University

Review: Full Adder: Truth Table

- A *Full-Adder* is a *Combinational circuit* that forms the arithmetic sum of three input bits.
- It consists of three inputs (z, x, y) and two outputs (*Carry*, *Sum*) as shown.

z	x	y	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth Table

xy z	00	01	11	10
0		1		1
1	1		1	

$$s = x \oplus y \oplus z$$

xy z	00	01	11	10
0			1	
1		1	1	1

$$c = xy + xz + yz = xy + z(x \oplus y)$$

Karnaugh maps

Review: Full Adder: Architecture

Entity Declaration

```
ENTITY full_adder IS
    PORT (x, y, z:      IN std_logic;
          Sum, Carry:   OUT std_logic
    ); END full_adder;
```

Optional Entity END **name**;

Architecture Declaration

```
ARCHITECTURE full_adder_arch_1 OF full_adder IS
BEGIN

    Sum <= ( ( x XOR y ) XOR z );

    Carry <= (( x AND y ) OR (z AND (x AND y)));

END full_adder_arch_1;
```

Optional Architecture END **name**;

Review: SIGNAL: Scheduled Event



- **SIGNAL**

Like variables in a programming language such as C, signals can be assigned values, e.g. 0, 1


- **However, SIGNALs also have an associated time value**

A signal receives a value at a specific point in time and retains that value until it receives a new value at a future point in time (**i.e. scheduled event**)


- The **waveform of the signal** is a sequence of values assigned to a signal over time

- **For example**
 
`wave <= '0', '1' after 10 ns, '0' after 15 ns, '1' after 25 ns;`



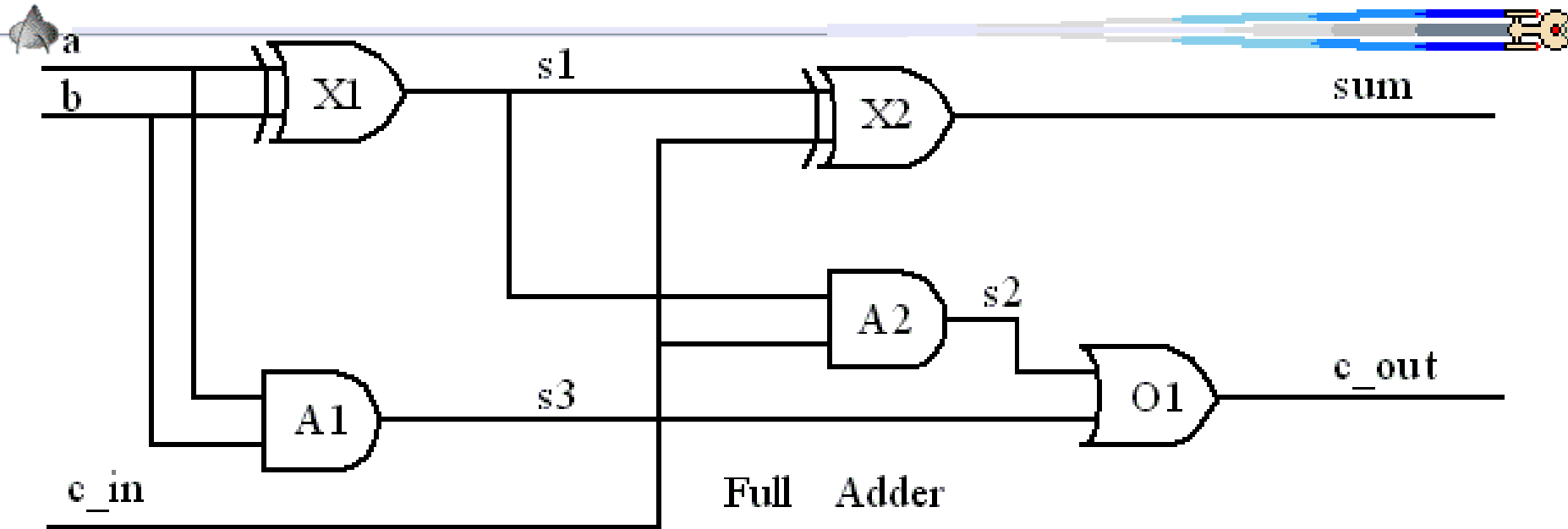Review: Full Adder: Architecture with Delay



ARCHITECTURE **full_adder_arch_2** OF **full_adder** IS

SIGNAL S1, S2, S3: std_logic;

BEGIN

s1 <= (**a** XOR **b**) after 15 ns;

s2 <= (**c_in** AND **s1**) after 5 ns;

s3 <= (**a** AND **b**) after 5 ns;

Sum <= (**s1** XOR **c_in**) after 15 ns;

Carry <= (**s2** OR **s3**) after 5 ns;

END;

Signals (like wires) are not PORTs they do not have direction (i.e. IN, OUT)

Signal order: Does it matter? No

```
ARCHITECTURE full_adder_arch_2 OF full_adder IS
    SIGNAL S1, S2, S3: std_logic;
BEGIN
    s1    <= ( a XOR b )      after 15 ns;
    s2    <= ( c_in AND s1 ) after 5 ns;
    s3    <= ( a AND b )      after 5 ns;
    Sum   <= ( s1 XOR c_in ) after 15 ns;
    Carry <= ( s2 OR s3 )     after 5 ns;
END;
```

```
ARCHITECTURE full_adder_arch_3 OF full_adder IS
    SIGNAL S1, S2, S3: std_logic;
BEGIN
    Carry <= ( s2 OR s3 )     after 5 ns;
    Sum   <= ( s1 XOR c_in ) after 15 ns;
    s3    <= ( a AND b )      after 5 ns;
    s2    <= ( c_in AND s1 ) after 5 ns;
    s1    <= ( a XOR b )      after 15 ns;
END;
```

No,
this
is not
C!

Net-
lists
have
same
beha-
vior
&
parall
el

Delta Delay


- **Default signal assignment propagation delay if no delay is explicitly prescribed**
 - **VHDL signal assignments do not take place immediately**
 - **Delta is an infinitesimal VHDL time unit so that all signal assignments can result in signals assuming their values at a future time**
 - **E.g.**

```
Output <= NOT Input;  
-- Output assumes new value in one delta cycle
```
- **Supports a model of concurrent VHDL process execution**
 - **Order in which processes are executed by simulator does not affect simulation output**

Delta Delay

An Example with Delta Delay

- What is the behavior of C?

 

Using delta delay scheduling

<u>Time</u>	<u>Delta</u>	<u>Event</u>
0 ns	1	IN: 1->0 eval INVERTER
	2	A: 0->1 eval NAND, AND
	3	B: 1->0 C: 0->1 eval AND
	4	C: 1->0
1 ns		

Inertial Delay


- Provides for specification propagation delay and input pulse width, i.e. 'inertia' of output:

```
target <= [REJECT time_expression] INERTIAL waveform;
```


- Inertial delay is default and REJECT is optional :

```
Output <= NOT Input AFTER 10 ns;  

 -- Propagation delay and minimum pulse width are 10ns
```



 
Inverter model: lowpass filter (inertial)




Transport Delay

- Transport delay must be explicitly specified
 - I.e. keyword “TRANSPORT” must be used
- Signal will assume its new value after specified delay
 
```
-- TRANSPORT delay example
Output <= TRANSPORT NOT Input AFTER 10 ns;
```



Inertial and Transport Delay

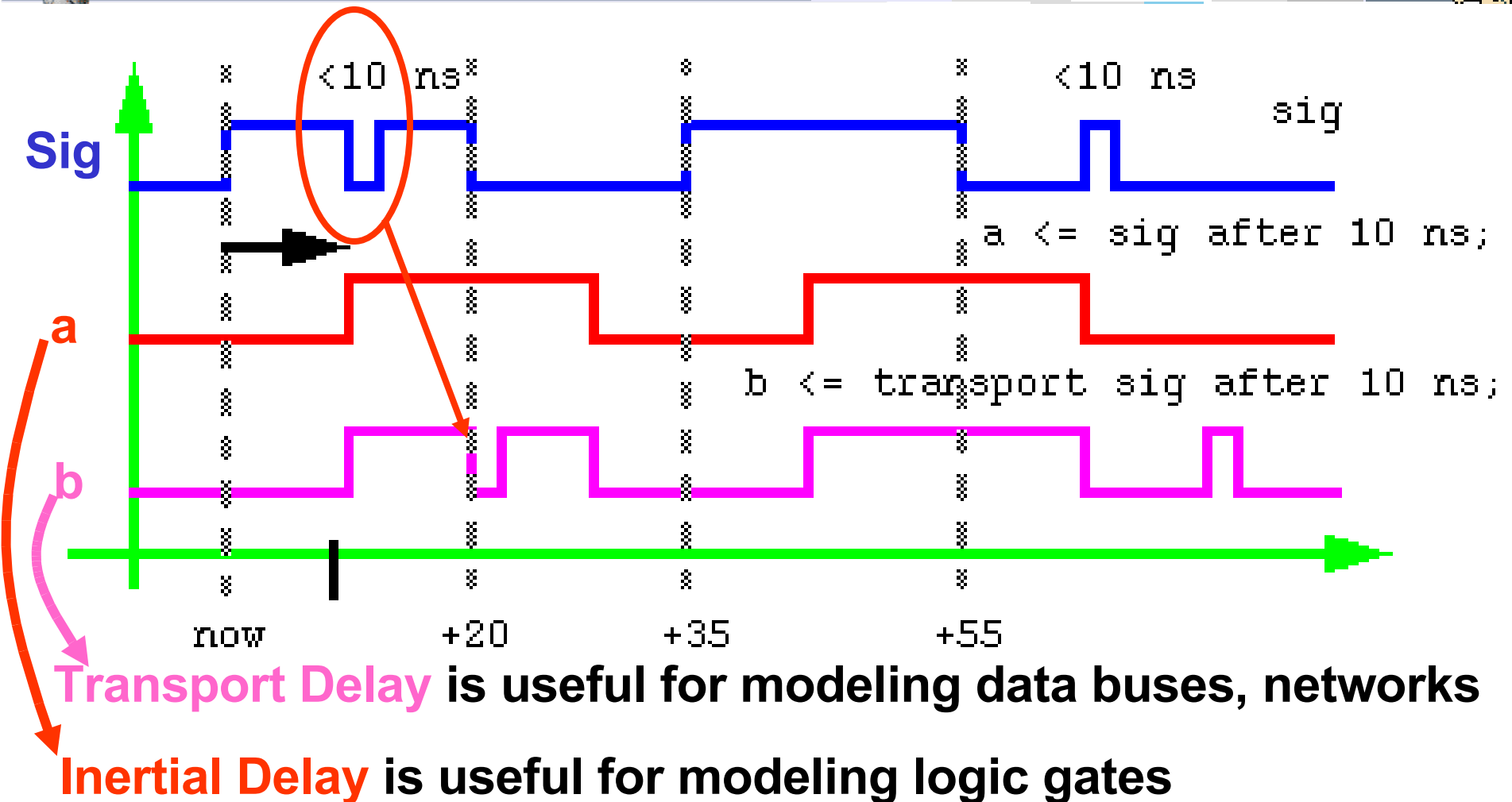

Combinatorial Logic Operators




#Transistors

2	NOT	$z \leq \text{NOT } (x); \quad z \leq \text{NOT } x;$
$2+2i$	AND	$z \leq x \text{ AND } y;$
$2i$	NAND	$z \leq \text{NOT } (x \text{ AND } y);$
$2+2i$	OR	$z \leq x \text{ OR } y;$
$2i$	NOR	$z \leq \text{NOT } (x \text{ OR } y);$
10	XOR	$z \leq (x \text{ and NOT } y) \text{ OR } (\text{NOT } x \text{ AND } y);$ $z \leq (x \text{ AND } y) \text{ NOR } (x \text{ NOR } y); \text{ --AOI}$
12	XNOR	$z \leq (x \text{ and } y) \text{ OR } (\text{NOT } x \text{ AND NOT } y);$ $z \leq (x \text{ NAND } y) \text{ NAND } (x \text{ OR } y); \text{ --OAI}$

Footnote: ($i=\#$ inputs) We are only referring to CMOS static transistor ASIC gate designs
Exotic XOR designs can be done in 6 (J. W. Wang, IEEE J. Solid State Circuits, 29, July 1994)

Std_logic AND: Un-initialized value

 

NOT	0	1	U
	1	0	U

AND	0	1	U
0	0	0	0
1	0	1	U
U	0	U	U

0 AND <anything> is 0


0 NAND <anything> is 1

OR	0	1	U
0	0	1	U
1	1	1	1
U	U	1	U

1 OR <anything> is 1

1 NOR <anything> is 0

SR Flip-Flop (Latch)

 


NOR

R	S	Q_{n+1}
0	0	Q_n
0	1	1
1	0	0
1	1	U

$Q \leq R \text{ NOR } NQ;$

$NQ \leq S \text{ NOR } Q;$

 


NAND

R	S	Q_{n+1}
0	0	U
0	1	1
1	0	0
1	1	Q_n


$Q \leq R \text{ NAND } NQ;$

$NQ \leq S \text{ NAND } Q;$


SR Flip-Flop (Latch)

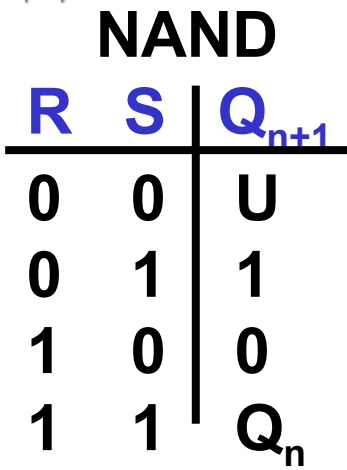

R	S	Q_{n+1}
0	0	U
0	1	1
1	0	0
1	1	Q_n

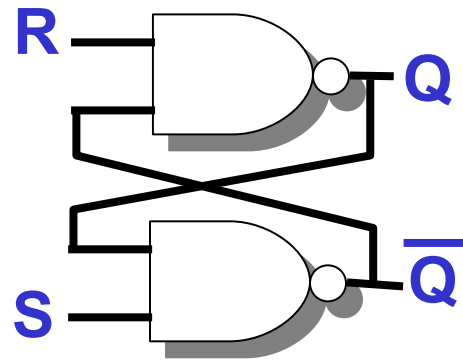


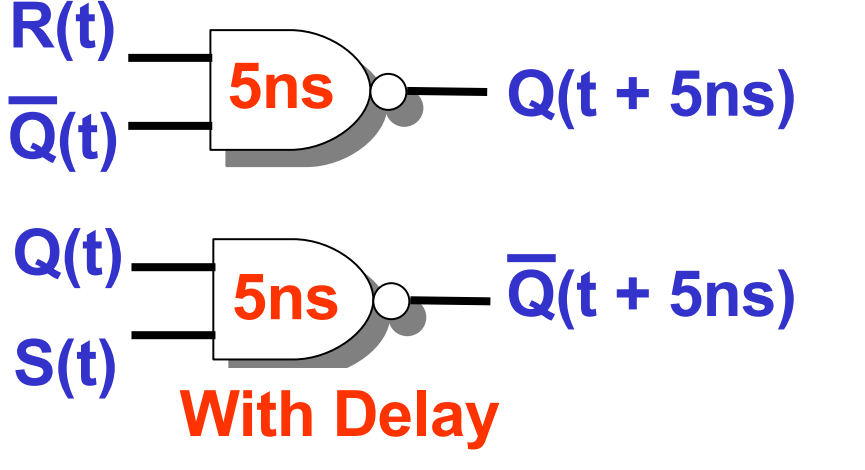Circuit diagram showing two NAND gates. The top NAND gate has inputs R and \bar{Q} , and output Q. The bottom NAND gate has inputs S and \bar{Q} , and output \bar{Q} . The outputs are cross-coupled.




Timing diagram showing the inputs R(t) and $\bar{Q}(t)$ to the top NAND gate, and Q(t) and S(t) to the bottom NAND gate. The outputs are Q(t + 5ns) and $\bar{Q}(t + 5ns)$. The delay of 5ns is indicated in red. The text "With Delay" is written in red.

 Example: R <= '1', '0' after 10ns, '1' after 30ns; S <= '1';



Std_logic AND: X Forcing Unknown Value

 

NOT	0	X	1	U
	1	X	0	U

AND	0	X	1	U
0	0	0	0	0
X	0	X	X	U
1	0	X	1	U
U	0	U	U	U

0 AND <anything> is 0

0 NAND <anything> is 1

OR	0	X	1	U
0	0	X	1	U
X	X	X	1	U
1	1	1	1	1
U	U	U	1	U


1 OR <anything> is 1

0 NOR <anything> is 1

The rising transition signal



$V_{CC}=5.5$ 25°C

 

Unknown
2.20 Volt
gap

Modeling logic gate values: std_ulogic



TYPE **std_ulogic** IS (-- Unresolved LOGIC

 'Z', -- High Impedance (Tri-State)

 '1', -- Forcing 1

 'H', -- Weak 1

 'X', -- Forcing Unknown: i.e. combining 0 and 1

 'W', -- Weak Unknown: i.e. combining H and L

 'L', -- Weak 0


 '0', -- Forcing 0

 'U', -- Un-initialized

 '-' , -- Don't care

);

**Example:
multiple drivers**

 


Multiple output drivers: Resolution Function



	U	X	0	L	Z	W	H	1	-
U	U	U	U	U	U	U	U	U	U
X	U	X	X	X	X	X	X	X	X
0	U	X	0	0	0	0	0	X	X
L									
Z									
W									
H									
1									
-	U	X	X	X	X	X	X	X	X

Suppose that
the first gate outputs a 1
the second gate outputs a 0
then
the mult-driver output is X
X: forcing unknown value by combining 1 and 0 together

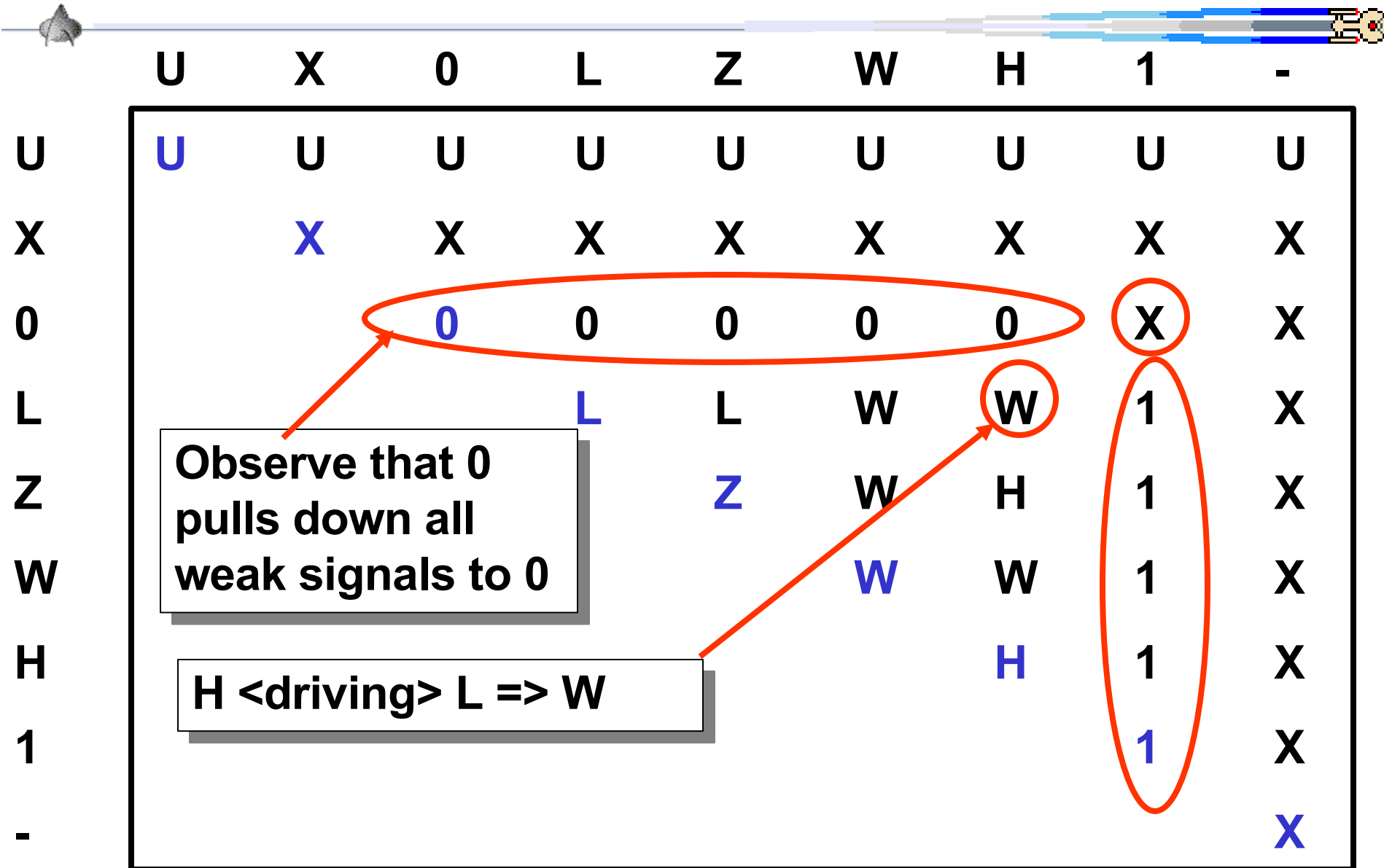Multiple output drivers: Resolution Function




	U	X	0	L	Z	W	H	1	-
U	U	U	U	U	U	U	U	U	U
X	X	X	X	X	X	X	X	X	X
0	0	0	0	0	0	0	0	X	X
L	L	L	L	L	L	W	W	1	X
Z	Z	Z	Z	Z	Z	W	H	1	X
W	W	W	W	W	W	W	W	1	X
H	H	H	H	H	H	H	H	1	X
1	1	1	1	1	1	1	1	1	X
-	-	-	-	-	-	-	-	-	X

Observe that 0 pulls down all weak signals to 0


H <driving> L => W

- Note the multi-driver resolution table is symmetrical

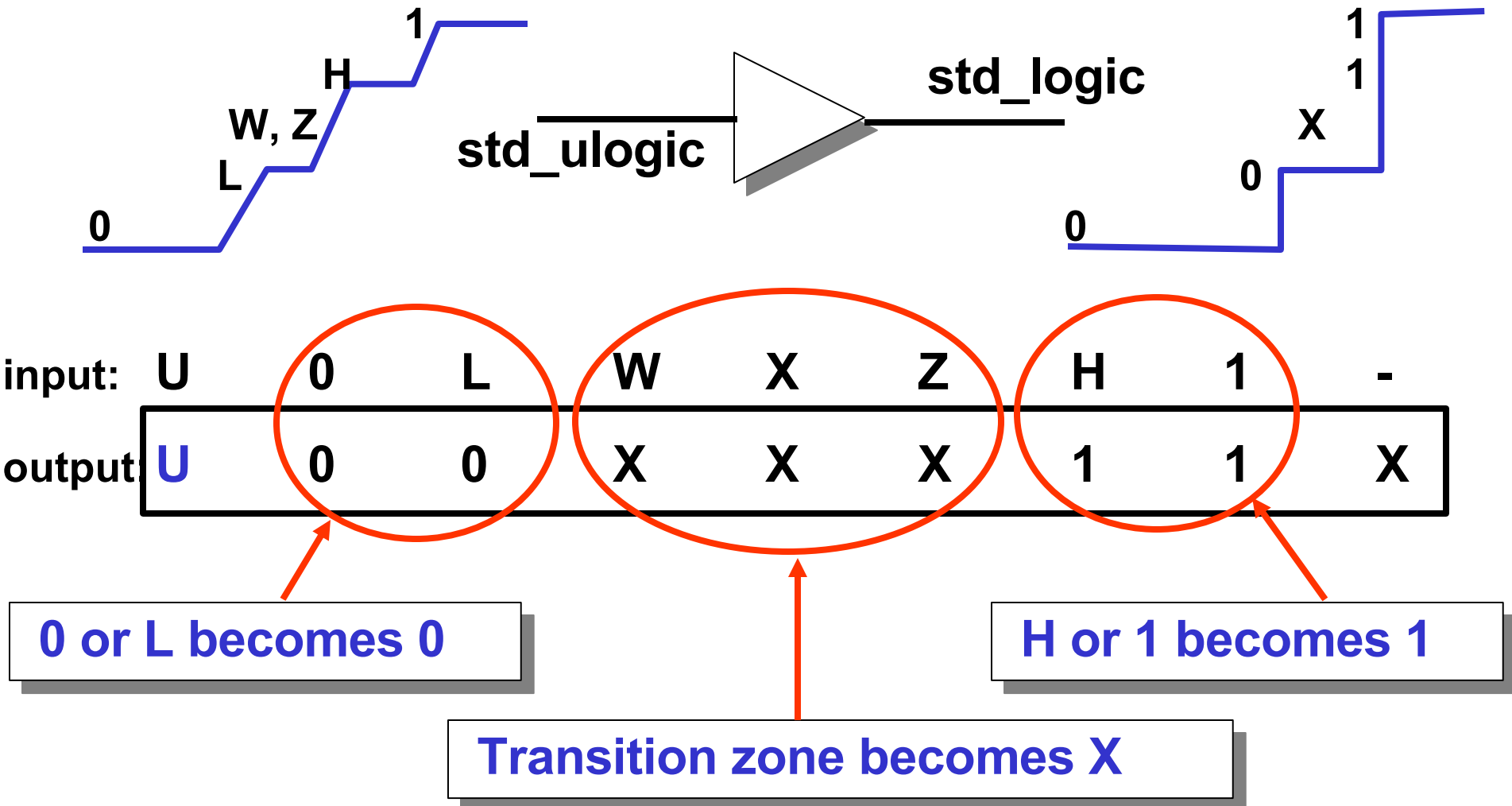Resolution Function: std_logic buffer gate



Resolving input: std_logic AND GATE

 

Process each input as an unresolved to resolved buffer.

Then process the gate as a standard logic gate { 0, X, 1, U }


For example, let's transform `z <= 'W' AND '1';`

`z <= 'W' AND '1';` -- convert `std_ulogic 'W'` to `std_logic 'X'`

`z <= 'X' AND '1';` -- now compute the `std_logic AND`

`z <= 'X';`

2-to-1 Multiplexor: with-select-when

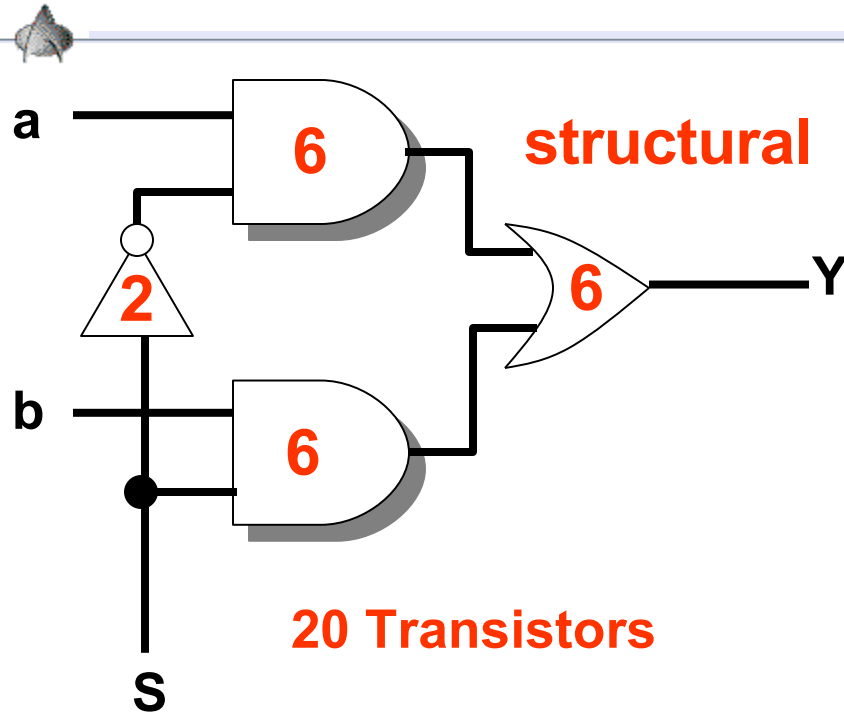


structural

20 Transistors

combinatorial logic
 
```
Y <= (a AND NOT s)
      OR
      (b AND s);
```



behavioral

Only
values
allowed

```
WITH s SELECT
  Y <= a WHEN '0',
      b WHEN '1';
```

or more general

```
WITH s SELECT
  Y <= a WHEN '0',
      b WHEN OTHERS;
```


OTHERS includes 1,U,L,W,X,H,Z

4-to-1 Multiplexor: with-select-when



Structural Combinatorial logic
 
```
Y <= sa OR sb OR sc OR sd;  
sa <= a AND ( NOT s(1) AND NOT s(0) );  
sb <= b AND ( NOT s(1) AND s(0) );  
sc <= c AND ( s(1) AND NOT s(0) );  
sd <= d AND ( s(1) AND s(0) );
```




As the complexity of the combinatorial logic **grows**, the SELECT statement, **simplifies** logic design but at a **loss** of structural information

```
WITH s SELECT  
Y <= a WHEN "00",  
    b WHEN "01",  
    c WHEN "10",  
    d WHEN OTHERS;
```

Note the comma after WHEN


behavioral

with-select-when: 2 to 4-line Decoder

 

Replace this
with a NOR,
then 26 total
transistors

 
SIGNAL **S**: std_logic_vector(1 downto 0);
SIGNAL **Y**: std_logic_vector(3 downto 0);



WITH **S** SELECT

```
Y <= "1000" WHEN "11",  
      "0100" WHEN "10",  
      "0010" WHEN "01",  
      "0001" WHEN OTHERS;
```

Tri-State buffer

 

```
ENTITY TriStateBuffer IS
    PORT(x:      IN      std_logic;
          y:      OUT     std_logic;
          oe:     IN      std_logic
    ); END;
```


ARCHITECTURE Buffer3 OF TriStateBuffer IS
BEGIN

WITH oe SELECT

y <= x WHEN '1', -- Enabled: y <= x;
 'Z' WHEN OTHERS; -- Disabled: output a tri-state

END;

Inverted Tri-State buffer

 

```
ENTITY TriStateBufferNot IS
    PORT(x:      IN      std_logic;
          y:      OUT     std_logic;
          oe:     IN      std_logic
    ); END;
```


ARCHITECTURE Buffer3 OF TriStateBufferNot IS
BEGIN

WITH oe SELECT

y <= NOT(x) WHEN '1', -- Enabled: y <= Not(x);
 'Z' WHEN OTHERS; -- Disabled

END;

ROM: 4 byte Read Only Memory

 

ROM: 4 byte Read Only Memory

ENTITY **rom_4x1** IS

PORT(**A**: IN std_logic_vector(1 downto 0);

OE: IN std_logic; -- **Tri-State Output**

D: OUT std_logic

); END;

ARCHITECTURE **rom_4x1_arch** OF **rom_4x1** IS

SIGNAL **ROMout**: std_logic;

BEGIN

BufferOut: **TriStateBuffer** PORT MAP(**ROMout**, **D**, **OE**);

WITH **A** SELECT

ROMout <= '1' WHEN "00",

'0' WHEN "01",

'0' WHEN "10",

'1' WHEN "11";

Component Instance

**Component
declaration
name**

Component Declaration/Instance relationship

ARCHITECTURE **rom_4x1_arch** OF **rom_4x1** IS

COMPONENT **TriStateBuffer**

PORT (**x**: IN std_logic; **y**: OUT std_logic, **oe**: IN std_logic);
END COMPONENT;

Component Declaration

SIGNAL **ROMout**: std_logic;
BEGIN

Colon (:) says make a
Component Instance

BufferOut: **TriStateBuffer** PORT MAP(**ROMout**, **D**, **OE**);


WITH **A** SELECT

ROMout <= '1' WHEN "00",
 '0' WHEN "01",
 '0' WHEN "10",
 '1' WHEN "11";

Component Instance
Name: *BufferOut*

END;

Component Port relationship

 

OE → IN → oe → IN

D → OUT → y → OUT

COMPONENT **TriStateBuffer**

PORT (**x**: IN std_logic; **y**: OUT std_logic, **oe**: IN std_logic);

END COMPONENT;

BufferOut: **TriStateBuffer** PORT MAP(**ROMout**, **D**, **OE**);

ENTITY **rom_4x1** IS


PORT(**A**: IN std_logic_vector(1 downto 0);

OE: IN std_logic; -- Tri-State Output

D: OUT std_logic


); END;

Assignment #2 (Part 1 of 3)

 

- 1) Assume each gate is 5 ns delay for the above circuit.
 - (a) Write entity-architecture for a inertial model
 - (b) Given the following waveform, draw, R, S, Q, NQ (**inertial**)
R <= '1', '0' after 25 ns, '1' after 30 ns, '1' after 50 ns;
S <= '0', '1' after 20 ns, '0' after 35 ns, '1' after 50 ns;
 - (c) Repeat (b) but now assume each gate is 20 ns delay
 - (d) Write entity-architecture for a transport model
 - (e) Given the waveform in (b) draw, R, S, Q, NQ (**transport**)

Assignment #2 (Part 2 of 3)

 

(2) Given the above two tri-state buffers connected together (assume transport model of 5ns per gate), draw **X**, **Y**, **F**, **a**, **b**, **G** for the following input waveforms:

X <= '1', '0' after 10 ns, 'X' after 20 ns, 'L' after 30 ns, '1' after 40 ns;
Y <= '0', 'L' after 10 ns, 'W' after 20 ns, '0' after 30 ns, 'Z' after 40 ns;
F <= '0', '1' after 10 ns, '0' after 50 ns;

Assignment #2 (Part 3 of 3)



3) Write **(no programming)** a entity-architecture for a **1-bit** ALU. The input will consist of **x**, **y**, **C_{in}**, **f** and the output will be **S** and **C_{out}**. Make **components** for 1-bit add/sub. The input function **f** (with-select) will enable the following operations:

<u>function f</u>	<u>ALU bit operation</u>
--------------------------	--------------------------

000	$S = 0; C_{out} = 0$
-----	----------------------

001	$S = x$
-----	---------

010	$S = y; C_{out} = 1;$
-----	-----------------------

011	$S = C_{in}; C_{out} = x$
-----	---------------------------

100	$S = x \text{ OR } y; C_{out} = x;$
-----	-------------------------------------

101	$S = x \text{ AND } y; C_{out} = x;$
-----	--------------------------------------

110	$(C_{out}, S) = x + y + C_{in};$ (component)
-----	---

111	$(C_{out}, S) = \text{full subtractor}$ (component)
-----	--

